
Home | Electronic Store | **Electronic Blog** | Electronic Schematics | Tutorials | Downloads | Contact

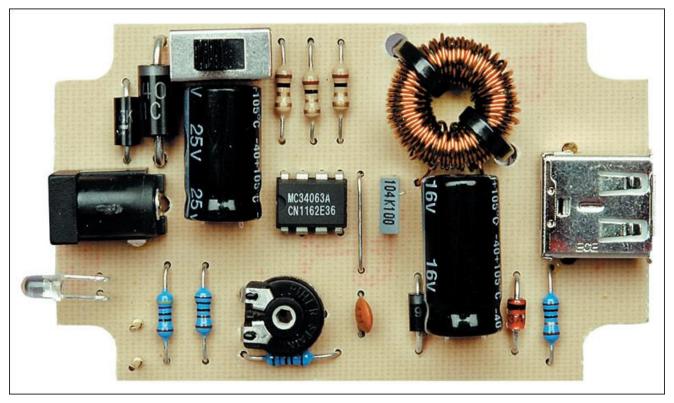






iPOD - MP3 Player Charger


Ads by Google Digital Design Circuit DIY Project Circuit PCB Electronic Circuit


Portable iPod charger that you can use while away from your computer. The circuit is based around an MC34063 switchmode regulator. This has high efficiency so that there is very little heat produced inside the box, even when delivering its maximum output current. The circuit is more complicated than if we used a 7805 3-terminal regulator but since the input voltage could be 15V DC or more, the voltage dissipation in such a regulator could be 5W or more at 500mA. and 5W is far too much for a 7805, even with quite a large heatsink.

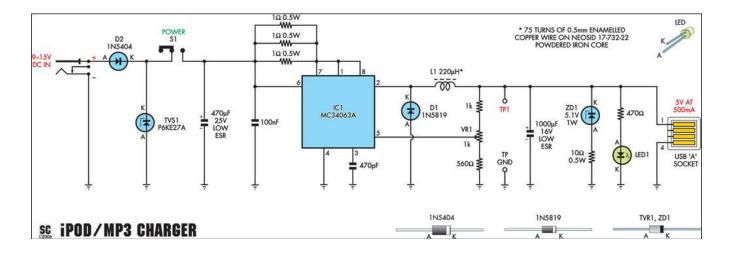

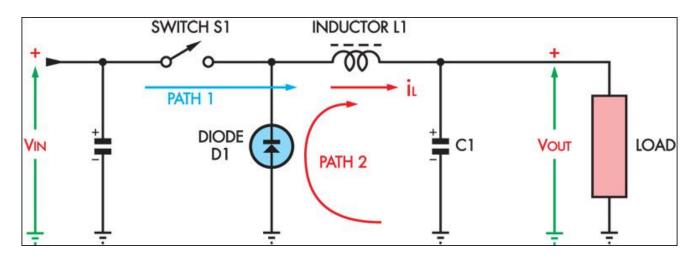

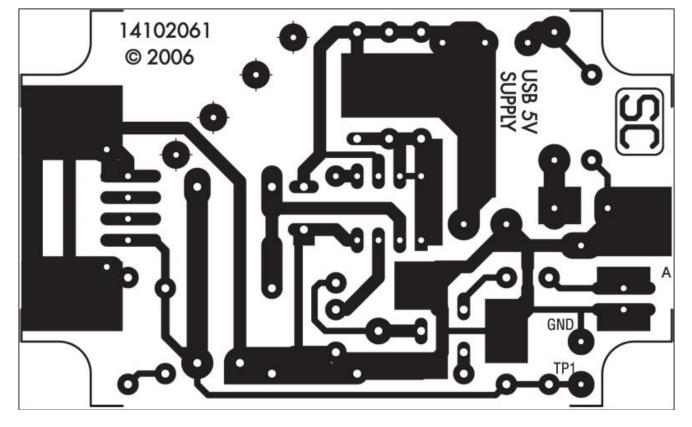

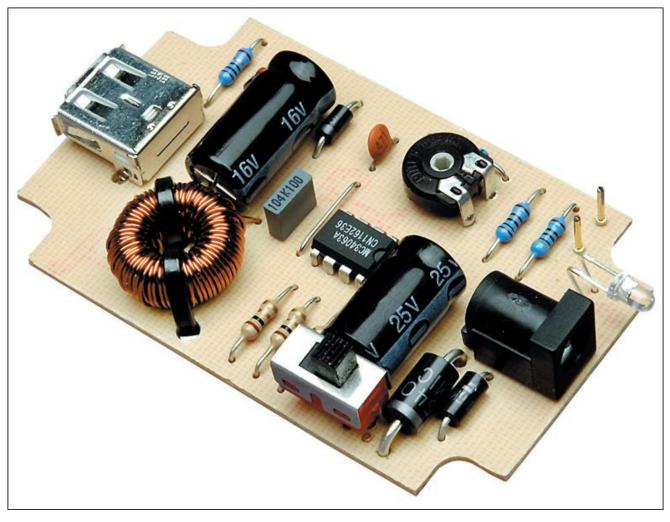

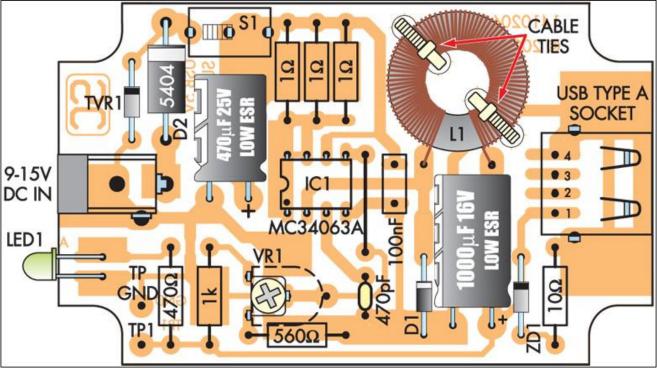

**Related Links** 

- Accurate LC Meter
- 60MHz Frequency Meter / Counter
- PIC Volt Ampere Meter
- 1Hz 2MHz Function Generator
- Accurate 0-500MHz RF Power Meter
- PIC Dual Temperature Meter
- BA1404 HI-FI Stereo FM Transmitter
- BH1417 Stereo PLL FM Transmitter
- 500mW FM / VHF Transmitter Amplifier / Booster
- 50mW BH1417 Stereo PLL FM Transmitter
- Phone FM Transmitter
- TV Transmitter with Audio
- 5 Watt FM Amplifier
- TDA7000 FM Receiver / TV Tuner / Aircraft Receiver
- NJM2035 HI-FI Stereo Encoder / Multiplexer
- USB IO Board

## **Downloads**

Ads by Google Digital Design Circuit DIY Project Circuit PCB Electronic Circuit

## iPOD - MP3 Player Charger - Link



Build your own LC Meter and start making your own coils and inductors. This LC Meter allows to measure incredibly small inductances making it perfect tool for making all types of RF coils. LC Meter can measure inductances starting from 10nH - 1000nH, 1uH - 1000uH, 1mH - 100mH and capacitances from 0.1pF up to 900nF. The circuit includes an auto ranging and "Zero Out" function to make sure the readings are as accurate as possible ... [more]

Electronics-DIY.com  $\ @$  2002-2011. All Rights Reserved.